

Homework 3

Problem 1. Consider a balanced, three-phase capacitive circuit, where each leg has Capacitance C with effective series resistance, R . Denote the voltages and currents across the RC combination as v_a , v_b , v_c and i_a , i_b , i_c . Derive corresponding expressions for the d and q-axis components.

Problem 2. The dynamics of a linear balanced-three phase inductive circuit in the $\alpha\beta$ domain are given by:

$$\begin{aligned} v_\alpha &= (L - M) \frac{di_\alpha}{dt} \\ v_\beta &= (L - M) \frac{di_\beta}{dt}. \end{aligned} \quad (1)$$

What are the corresponding dynamics in the abc domain?

Problem 3. In this problem, we will examine some dynamic attributes of a three-phase grid-forming (GFM) voltage-source inverter (VSI). The inverter includes a dc voltage source, v_{dc} , a hex-bridge converter, and an output inductive filter with inductance L_f and resistance R_f (these may also include line impedances, if any). We assume droop control is employed for voltage and frequency regulation. The system architecture with this control type is depicted in Fig. 2. The three-phase voltages corresponding to the external network and the inverter terminals are denoted by e_{abc} and v_{abc} , respectively. In the $\alpha\beta$ reference frame, we can represent the network and inverter-terminal voltages as:

$$\begin{cases} e_\alpha = \sqrt{2}E \cos \omega_e t \\ e_\beta = \sqrt{2}E \sin \omega_e t, \end{cases} \quad \begin{cases} v_\alpha = \sqrt{2}V \cos \omega_i t \\ v_\beta = \sqrt{2}V \sin \omega_i t. \end{cases} \quad (2)$$

Implicit in the definitions above is that the amplitudes of the two voltages are denoted by $\sqrt{2}E$, $\sqrt{2}V$; and frequencies are denoted by ω_e , ω_i . In what follows, we will also find it useful to define corresponding voltage phase angles by $\theta_e = \omega_e t$, $\theta_i = \omega_i t$, respectively. To facilitate analysis, we will reference the angle difference $\delta = \theta_i - \theta_e$ in subsequent developments. The inverter output currents (referred interchangeably as line currents) in the $\alpha\beta$ reference frame are denoted by i_α , i_β , respectively, and in the local dq reference frame by i_d , i_q , respectively. Figure 1 illustrates several of the quantities referenced above.

Now consider the implementation of droop control depicted in Fig. 2. At the core are the following linear trade-offs:

$$V = V_{\text{nom}} - m_q(\bar{Q} - Q^*), \quad (3a)$$

$$\omega_i = \omega_{\text{nom}} - m_p(\bar{P} - P^*), \quad (3b)$$

where \bar{P} , \bar{Q} are filtered active- and reactive-power values measured at the inverter terminals (we discuss this shortly), and m_q , m_p are determined by the voltage- and frequency-droop specifications. For instance, if we assume a 5% voltage droop and 0.5 Hz frequency droop while the inverters are running at rated power S_{rated} , then it follows that $m_q = 0.05V_{\text{nom}}/S_{\text{rated}}$ and $m_p = 2\pi 0.5 \text{ Hz}/S_{\text{rated}}$. To reject double-frequency pulsating components that arise from imbalances and switching ripple (which are inescapable in practical systems) from the power calculations, a low-pass (LP) filter is required. In this problem, we will assume a first-order LP filter. The dynamics of the filtered active- and reactive-power, denoted by \bar{P} and \bar{Q} , respectively, can be written as

$$\dot{\bar{P}} = \omega_c(\bar{P} - P), \quad \dot{\bar{Q}} = \omega_c(\bar{Q} - Q), \quad (4)$$

where ω_c is the cut-off frequency which typically ranges from several Hz to tens of Hz. In general, the LP filter will hinder control responsiveness as the filtered quantities are leveraged inside the droop controller. Therefore, the selection of the cut-off frequency, ω_c , is an important design choice and it presents an important trade-off between power-filtering performance and system-transient response. With these definitions in place, we see that the dynamics of the terminal voltage amplitude V and angle θ_i in (3) are given by:

$$\dot{V} = -m_q \dot{\bar{Q}} = m_q \omega_c (\bar{Q} - Q^*), \quad (5a)$$

$$\dot{\theta}_i = \omega_{\text{nom}} - m_p (\bar{P} - P^*). \quad (5b)$$

In subsequent developments, we will express the phase dynamics with the power angle δ as follows

$$\dot{\delta} = \omega_{\text{nom}} - \omega_e - m_p (\bar{P} - P^*). \quad (6)$$

Part (i). Let e_d, e_q correspond to the dq reference-frame representations of the external network voltage e_{abc} . Using an appropriate reference transformation, express e_d, e_q as a function of δ and E .

Part (ii) Derive the state-space model for the dynamics of i_d, i_q with inputs e_d, e_q .

Part (iii) Show that the instantaneous active and reactive power at the inverter terminals P, Q are given by

$$P = \frac{3}{2} \sqrt{2} V i_d, \quad Q = -\frac{3}{2} \sqrt{2} V i_q. \quad (7)$$

Part (iv) List down the dynamical equations for i_d, i_q, V, δ , and \bar{P} clearly indicating all parameters and inputs. This fifth-order model captures all dynamics of the GFM inverter with droop control. Note that the filtered reactive power is linearly related to the terminal voltage, and therefore, while we can recover it's dynamics, we will not carry it forward in the analysis.

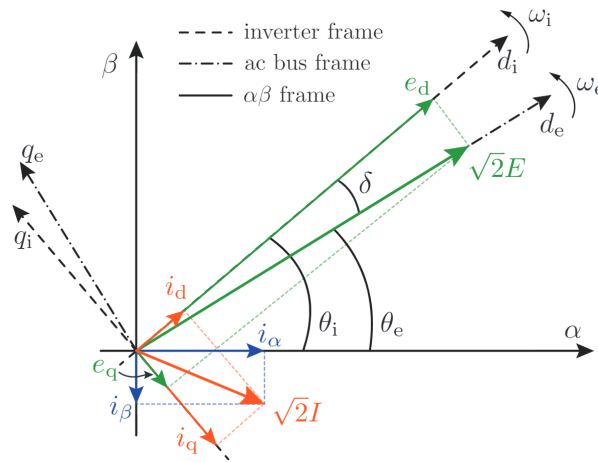


Figure 1: Illustrating frequently referenced voltage and current signals in pertinent reference frames.

Part (v) Show that the equilibria of the dynamics of the GFM inverter with droop control are obtained from the solution of the following nonlinear equations:

$$\omega_{\text{nom}} - \omega_e - m_p (\bar{P}_{\text{eq}} - P^*) = 0, \quad (8a)$$

$$V_{\text{eq}} - V_{\text{nom}} - m_q \left(\frac{3}{2} \sqrt{2} V_{\text{eq}} i_{q,\text{eq}} + Q^* \right) = 0, \quad (8b)$$

$$-\frac{R_f}{L_f} i_{d,\text{eq}} + \omega_i i_{q,\text{eq}} + \frac{\sqrt{2}}{L_f} (V_{\text{eq}} - E \cos \delta_{\text{eq}}) = 0, \quad (8c)$$

$$-\frac{R_f}{L_f} i_{q,\text{eq}} - \omega_i i_{d,\text{eq}} + \frac{\sqrt{2}}{L_f} (E \sin \delta_{\text{eq}}) = 0, \quad (8d)$$

$$\bar{P}_{\text{eq}} - \frac{3}{2} \sqrt{2} V_{\text{eq}} i_{d,\text{eq}} = 0, \quad (8e)$$

where $\delta_{\text{eq}}, V_{\text{eq}}$ are the terminal voltage amplitude and phase-angle equilibria corresponding to the voltage and phase dynamics; $i_{d,\text{eq}}, i_{q,\text{eq}}$ are the equilibrium values of the d and q axis current dynamics; and \bar{P}_{eq} is the equilibrium value of the filtered active power.

Part (vi) We will now derive a small-signal model for the dynamical model. The state vector of the small-signal model is defined as $\Delta x = [\Delta \delta, \Delta V, \Delta i_d, \Delta i_q, \Delta \bar{P}]^\top$. The dynamics of the small-signal model are obtained by linearizing the dynamical model you derived in **Part (iv)**. The small-signal model is compactly represented as $\Delta \dot{x} = A \Delta x$, where A is the Jacobian matrix of the nonlinear dynamical model evaluated for the equilibria referenced above. Write out the A matrix (25 entries) for this small-signal model.

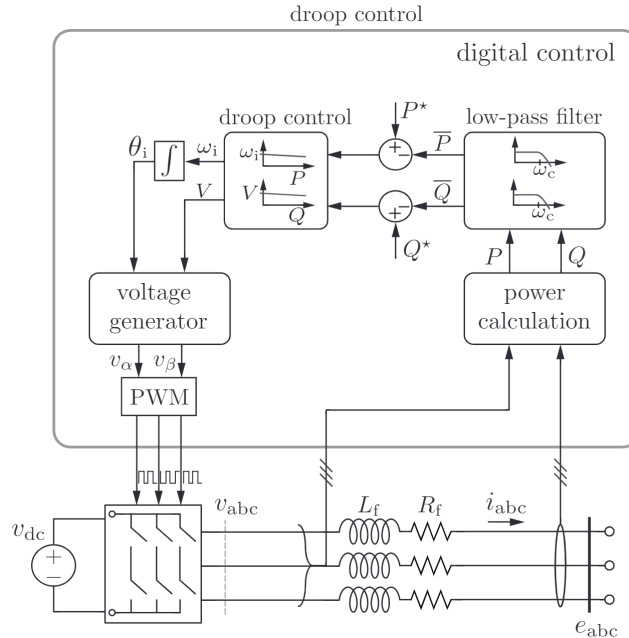


Figure 2: Voltage source inverter with droop controller. The “power calculation” block calculates the active- and reactive-power using (7), the “low-pass filter” block comprises two low-pass filters with cutoff frequency of ω_c , the “droop control” block denotes the droop relationships given in (3), and the “voltage generator” block generates the PWM modulation signals in the $\alpha\beta$ reference frame given corresponding polar-coordinate inputs.

Problem 4. Consider the half-bridge circuit with current control illustrated in Fig. 3. Suppose we employ the following PI compensator:

$$G_c(s) = k_p + k_i \frac{1}{s}. \quad (9)$$

Part (i) With appropriate feed-forward cancellation, show that you obtain the circuit in Fig. 4 in a local dq reference frame.

Part (ii) Show that the closed-loop response from the d and q -axis current references to currents are given by

$$H(s) = \frac{k_p + k_i/s}{(k_p + k_i/s) + (R + sL)}. \quad (10)$$

Part (iii) Prove that the closed-loop transfer function, $H(s)$, is first-order with time constant, τ ,

$$H(s) = \frac{1}{1 + \tau s}, \quad (11)$$

if and only if the time constant τ_c of the PI compensator, $\tau_c = \frac{k_p}{k_i}$, matches the time constant τ_f of the inductive output filter $\tau_f = \frac{L}{R}$.

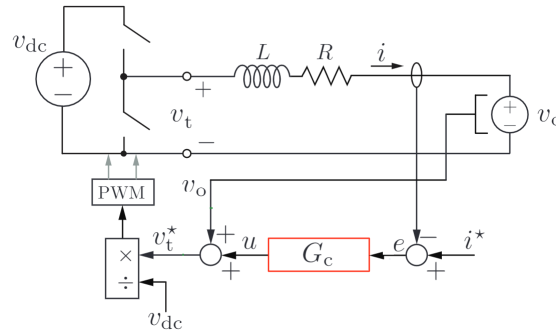


Figure 3: Voltage source half-bridge circuit with output RL filter.

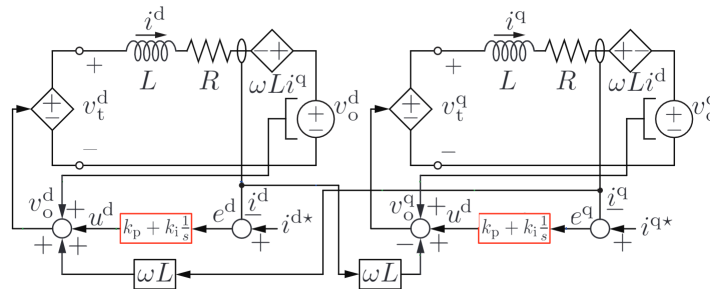


Figure 4: Voltage source half-bridge circuit with output RL filter in dq reference frame with feedforward cancellation.