

## HW 3

---

ARNAB DEY

Student ID: 5563169

Email: dey00011@umn.edu

### Problem 1

In case of a balanced three-phase capacitive circuit with effective series resistance  $R$ , we can get the following dynamics from KVL in time domain:

$$C \frac{d}{dt} \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix} - RC \frac{d}{dt} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix}. \quad (1)$$

We know that, for a vector  $[x_a \ x_b \ x_c]^T$  represented in 3-phase domain can be transformed to d-q axis (at an angle  $\theta_d$ ) with amplitude preservation in the following way:

$$\begin{bmatrix} x_d \\ x_q \end{bmatrix} = \frac{2}{3} \Gamma_{dq} \begin{bmatrix} x_a \\ x_b \\ x_c \end{bmatrix},$$

where,

$$\Gamma_{dq} = \begin{bmatrix} \cos \theta_d & \cos(\theta_d - \frac{2\pi}{3}) & \cos(\theta_d + \frac{2\pi}{3}) \\ -\sin \theta_d & -\sin(\theta_d - \frac{2\pi}{3}) & -\sin(\theta_d + \frac{2\pi}{3}) \end{bmatrix}.$$

The inverse transform can be shown to be:

$$\begin{bmatrix} x_a \\ x_b \\ x_c \end{bmatrix} = \Gamma_{dq}^T \begin{bmatrix} x_d \\ x_q \end{bmatrix}.$$

Let us derive  $\frac{d}{dt} \Gamma_{dq}^T$  first as it will be required later.

$$\begin{aligned} \frac{d}{dt} \Gamma_{dq}^T &= \dot{\theta}_d \begin{bmatrix} -\sin \theta_d & \cos \theta_d \\ -\sin(\theta_d - \frac{2\pi}{3}) & -\cos(\theta_d - \frac{2\pi}{3}) \\ -\sin(\theta_d + \frac{2\pi}{3}) & -\cos(\theta_d + \frac{2\pi}{3}) \end{bmatrix} \\ &= \dot{\theta}_d \Gamma_{dq}^T \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix}. \end{aligned}$$

Therefore, from Eq. 1,

$$\begin{aligned} &C \frac{d}{dt} \left( \Gamma_{dq}^T \begin{bmatrix} v_d \\ v_q \end{bmatrix} \right) - RC \frac{d}{dt} \left( \Gamma_{dq}^T \begin{bmatrix} i_d \\ i_q \end{bmatrix} \right) = \Gamma_{dq}^T \begin{bmatrix} i_d \\ i_q \end{bmatrix} \\ \Rightarrow &C \dot{\theta}_d \Gamma_{dq}^T \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} v_d \\ v_q \end{bmatrix} + C \Gamma_{dq}^T \begin{bmatrix} \dot{v}_d \\ \dot{v}_q \end{bmatrix} - RC \dot{\theta}_d \Gamma_{dq}^T \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i_d \\ i_q \end{bmatrix} - RC \Gamma_{dq}^T \begin{bmatrix} \dot{i}_d \\ \dot{i}_q \end{bmatrix} = \Gamma_{dq}^T \begin{bmatrix} i_d \\ i_q \end{bmatrix} \\ \Rightarrow &C \dot{\theta}_d \begin{bmatrix} -v_q \\ v_d \end{bmatrix} + C \begin{bmatrix} \dot{v}_d \\ \dot{v}_q \end{bmatrix} - RC \dot{\theta}_d \begin{bmatrix} -i_q \\ i_d \end{bmatrix} - RC \begin{bmatrix} \dot{i}_d \\ \dot{i}_q \end{bmatrix} = \begin{bmatrix} i_d \\ i_q \end{bmatrix} \\ \Rightarrow &C \left( \begin{bmatrix} \dot{v}_d \\ \dot{v}_q \end{bmatrix} - R \begin{bmatrix} \dot{i}_d \\ \dot{i}_q \end{bmatrix} \right) + C \dot{\theta}_d \begin{bmatrix} -v_q \\ v_d \end{bmatrix} - RC \dot{\theta}_d \begin{bmatrix} -i_q \\ i_d \end{bmatrix} = \begin{bmatrix} i_d \\ i_q \end{bmatrix}. \end{aligned}$$

Therefore, the dynamics in dq domain can be written as:

$$\begin{aligned} C \frac{d}{dt} (v_d - i_d R) - C \dot{\theta}_d v_q + RC \dot{\theta}_d i_q &= i_d, \\ C \frac{d}{dt} (v_q - i_q R) + C \dot{\theta}_d v_d - RC \dot{\theta}_d i_d &= i_q. \end{aligned}$$

## Problem 2

We know that for any vector  $[x_a \ x_b \ x_c]^T$  in 3-phase time domain can be transformed to  $\alpha - \beta$  domain, with amplitude preservation, as follows:

$$\begin{bmatrix} x_\alpha \\ x_\beta \end{bmatrix} = T \begin{bmatrix} x_a \\ x_b \\ x_c \end{bmatrix},$$

where,

$$T = \frac{2}{3} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix}.$$

The inverse transform can be obtained using pseudo-inverse of  $T$ . We can use singular value decomposition (SVD) to derive the pseudo-inverse of  $T$ . Using MATLAB, we get the following SVD components:

$$T = USV^T,$$

where,

$$U = \begin{bmatrix} 0 & -1 \\ -1 & 0 \end{bmatrix},$$

$$S = \begin{bmatrix} \frac{\sqrt{2}}{\sqrt{3}} & 0 \\ 0 & \frac{\sqrt{2}}{\sqrt{3}} \end{bmatrix},$$

$$V = \begin{bmatrix} 0 & -\frac{\sqrt{2}}{\sqrt{3}} \\ -\frac{1}{\sqrt{2}} & \frac{\sqrt{2}}{2\sqrt{3}} \\ \frac{1}{\sqrt{2}} & \frac{\sqrt{2}}{2\sqrt{3}} \end{bmatrix}.$$

Therefore, pseudo-inverse of  $T$  is given by:

$$\begin{aligned} T^+ &= VS^{-1}U^T \\ &= \begin{bmatrix} 1 & 0 \\ -\frac{1}{2} & \frac{\sqrt{3}}{2} \\ -\frac{1}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix}. \end{aligned}$$

Therefore,

$$\begin{bmatrix} x_a \\ x_b \\ x_c \end{bmatrix} = T^+ \begin{bmatrix} x_\alpha \\ x_\beta \end{bmatrix}.$$

Now, the dynamics given in the question is:

$$\begin{aligned} \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} &= (L - M) \frac{d}{dt} \begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} \\ \Rightarrow T \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix} &= (L - M) \frac{d}{dt} \left( T \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} \right) \\ \Rightarrow T^+ T \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix} &= (L - M) T^+ T \frac{d}{dt} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} \\ \Rightarrow \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix} &= (L - M) \frac{d}{dt} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix}. \end{aligned}$$

This is the corresponding dynamics in the  $abc$ -domain.

### Problem 3

In the  $\alpha - \beta$  reference frame, the network and the inverter terminal voltages are given as:

$$\begin{aligned} e_\alpha &= \sqrt{2}E \cos \omega_e t \\ e_\beta &= \sqrt{2}E \sin \omega_e t, \end{aligned} \quad (2)$$

and

$$\begin{aligned} v_\alpha &= \sqrt{2}V \cos \omega_i t \\ v_\beta &= \sqrt{2}V \sin \omega_i t. \end{aligned} \quad (3)$$

The reference angle difference is given by:

$$\delta = \theta_i - \theta_e, \quad (4)$$

where,  $\theta_i = \omega_i t$  and  $\theta_e = \omega_e t$ . The droop control equations are given by:

$$\begin{aligned} V &= V_{nom} - m_q(\bar{Q} - Q^*), \\ \omega_i &= \omega_{nom} - m_p(\bar{P} - P^*), \end{aligned} \quad (5)$$

where the  $\bar{P}, \bar{Q}$  are the filtered active and reactive powers and their dynamics are given by:

$$\begin{aligned} \dot{\bar{P}} &= \omega_c(\bar{P} - P), \\ \dot{\bar{Q}} &= \omega_c(\bar{Q} - Q), \end{aligned} \quad (6)$$

where  $P, Q$  are instantaneous active and reactive power at the inverter terminal. Therefore, from Eq. 5 and Eq. 6, we can derive that,

$$\begin{aligned} \dot{V} &= -m_q(\dot{\bar{Q}}) \\ &= -m_q\omega_c(\bar{Q} - Q), \\ \dot{\theta}_i &= \omega_i = \omega_{nom} - m_p(\bar{P} - P^*), \\ \dot{\delta} &= \omega_{nom} - \omega_e - m_p(\bar{P} - P^*). \end{aligned} \quad (7)$$

#### Problem 3.i

In the d-q reference frame, as shown in Fig. (1) in the question,

$$\begin{aligned} \begin{bmatrix} e_d \\ e_q \end{bmatrix} &= \begin{bmatrix} \cos \theta_i & \sin \theta_i \\ -\sin \theta_i & \cos \theta_i \end{bmatrix} \begin{bmatrix} e_\alpha \\ e_\beta \end{bmatrix} \\ &= \sqrt{2}E \begin{bmatrix} \cos \theta_i & \sin \theta_i \\ -\sin \theta_i & \cos \theta_i \end{bmatrix} \begin{bmatrix} \cos \theta_e \\ \sin \theta_e \end{bmatrix} \\ &= \sqrt{2}E \begin{bmatrix} \cos \theta_i \cos \theta_e + \sin \theta_i \sin \theta_e \\ -\cos \theta_e \sin \theta_i + \sin \theta_e \cos \theta_i \end{bmatrix} \\ &= \begin{bmatrix} \sqrt{2}E \cos \delta \\ -\sqrt{2}E \sin \delta \end{bmatrix}. \end{aligned} \quad (8)$$

Before proceeding, let us derive  $v_d, v_q$  also, which will be required later.

$$\begin{aligned} \begin{bmatrix} v_d \\ v_q \end{bmatrix} &= \begin{bmatrix} \cos \theta_i & \sin \theta_i \\ -\sin \theta_i & \cos \theta_i \end{bmatrix} \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} \\ &= \sqrt{2}V \begin{bmatrix} \cos \theta_i & \sin \theta_i \\ -\sin \theta_i & \cos \theta_i \end{bmatrix} \begin{bmatrix} \cos \theta_i \\ \sin \theta_i \end{bmatrix} \\ &= \begin{bmatrix} \sqrt{2}V \\ 0 \end{bmatrix}. \end{aligned} \quad (9)$$

### Problem 3.ii

We know that, for a vector  $[x_a \ x_b \ x_c]^T$  represented in 3-phase domain can be transformed to d-q axis (at an angle  $\theta_i$ ) with amplitude preservation in the following way:

$$\begin{bmatrix} x_d \\ x_q \end{bmatrix} = \frac{2}{3} \Gamma_{dq} \begin{bmatrix} x_a \\ x_b \\ x_c \end{bmatrix},$$

where,

$$\Gamma_{dq} = \begin{bmatrix} \cos \theta_i & \cos(\theta_i - \frac{2\pi}{3}) & \cos(\theta_i + \frac{2\pi}{3}) \\ -\sin \theta_i & -\sin(\theta_i - \frac{2\pi}{3}) & -\sin(\theta_i + \frac{2\pi}{3}) \end{bmatrix}.$$

The inverse transform can be shown to be:

$$\begin{bmatrix} x_a \\ x_b \\ x_c \end{bmatrix} = \Gamma_{dq}^T \begin{bmatrix} x_d \\ x_q \end{bmatrix}.$$

Let us derive  $\frac{d}{dt} \Gamma_{dq}^T$  first as it will be required later.

$$\begin{aligned} \frac{d}{dt} \Gamma_{dq}^T &= \dot{\theta}_i \begin{bmatrix} -\sin \theta_i & \cos \theta_i \\ -\sin(\theta_i - \frac{2\pi}{3}) & -\cos(\theta_i - \frac{2\pi}{3}) \\ -\sin(\theta_i + \frac{2\pi}{3}) & -\cos(\theta_i + \frac{2\pi}{3}) \end{bmatrix} \\ &= \dot{\theta}_i \Gamma_{dq}^T \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix}. \end{aligned}$$

Now, using KVL in the inverter, RL, and network model, we get:

$$\begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix} = R_f \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} + L_f \frac{d}{dt} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} + \begin{bmatrix} e_a \\ e_b \\ e_c \end{bmatrix}.$$

Transforming all the vectors to d-q axis, we get:

$$\begin{aligned} \Gamma_{dq}^T \begin{bmatrix} v_d \\ v_q \end{bmatrix} &= R_f \Gamma_{dq}^T \begin{bmatrix} i_d \\ i_q \end{bmatrix} + L_f \frac{d}{dt} \left( \Gamma_{dq}^T \begin{bmatrix} i_d \\ i_q \end{bmatrix} \right) + \Gamma_{dq}^T \begin{bmatrix} e_d \\ e_q \end{bmatrix} \\ \Rightarrow \begin{bmatrix} v_d \\ v_q \end{bmatrix} &= R_f \begin{bmatrix} i_d \\ i_q \end{bmatrix} + L_f \dot{\theta}_i \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i_d \\ i_q \end{bmatrix} + L_f \begin{bmatrix} \dot{i}_d \\ \dot{i}_q \end{bmatrix} + \begin{bmatrix} e_d \\ e_q \end{bmatrix} \\ \Rightarrow \begin{bmatrix} \dot{i}_d \\ \dot{i}_q \end{bmatrix} &= -\frac{R_f}{L_f} \begin{bmatrix} i_d \\ i_q \end{bmatrix} - \dot{\theta}_i \begin{bmatrix} -i_q \\ i_d \end{bmatrix} + \frac{1}{L_f} \begin{bmatrix} v_d \\ v_q \end{bmatrix} - \frac{1}{L_f} \begin{bmatrix} e_d \\ e_q \end{bmatrix} \\ \Rightarrow \begin{bmatrix} \dot{i}_d \\ \dot{i}_q \end{bmatrix} &= \begin{bmatrix} -\frac{R_f}{L_f} & \dot{\theta}_i \\ -\dot{\theta}_i & -\frac{R_f}{L_f} \end{bmatrix} \begin{bmatrix} i_d \\ i_q \end{bmatrix} + \frac{1}{L_f} \begin{bmatrix} \sqrt{2}V - e_d \\ -e_q \end{bmatrix}. \end{aligned} \tag{10}$$

### Problem 3.iii

Using 9, we can derive the instantaneous active power at the inverter terminal as follows:

$$\begin{aligned} P &= \frac{3}{2} (v_d i_d + v_q i_q) \\ &= \frac{3}{2} (\sqrt{2}V i_d). \end{aligned} \tag{11}$$

Similarly the instantaneous reactive power is:

$$\begin{aligned} Q &= \frac{3}{2} (-v_d i_q + v_q i_d) \\ &= -\frac{3}{2} \sqrt{2}V i_q. \end{aligned}$$

### Problem 3.iv

$$\begin{aligned}
\dot{\delta} &= f_{\delta} = \omega_{nom} - \omega_e - m_p(\bar{P} - P^*) \\
\dot{V} &= f_v = -m_q\omega_c(\bar{Q} - Q) \\
&= -m_q\omega_c\left(\frac{V_{nom} - V}{m_q} + Q^*\right) + m_q\omega_c Q \\
&= \omega_c V - \omega_c V_{nom} - m_q\omega_c\left(\frac{3}{2}\sqrt{2}Vi_q + Q^*\right) \\
\dot{i}_d &= f_{i_d} = -\frac{R_f}{L_f}i_d + \dot{\theta}_i i_q + \frac{1}{L_f}(\sqrt{2}V - e_d) \\
&= -\frac{R_f}{L_f}i_d + \omega_i i_q + \frac{\sqrt{2}}{L_f}(V - E \cos \delta) \\
\dot{i}_q &= f_{i_q} = -\dot{\theta}_i i_d - \frac{R_f}{L_f}i_q + \frac{1}{L_f}(-e_q) \\
&= -\omega_i i_d - \frac{R_f}{L_f}i_q + \frac{\sqrt{2}}{L_f}(E \sin \delta) \\
\dot{\bar{P}} &= f_{\bar{P}} = \omega_c(\bar{P} - P) = \omega_c\left(\bar{P} - \frac{3}{2}\sqrt{2}Vi_d\right)
\end{aligned} \tag{12}$$

### Problem 3.v

In equilibria,

$$\begin{aligned}
\dot{\delta} &= 0 \\
\dot{V} &= 0 \\
\dot{i}_d &= 0 \\
\dot{i}_q &= 0 \\
\dot{\bar{P}} &= 0.
\end{aligned}$$

Therefore, from 12, we get:

$$\begin{aligned}
\omega_{nom} - \omega_c - m_p(\bar{P}_{eq} - P^*) &= 0, \\
V_{eq} - V_{nom} - m_q\left(\frac{3}{2}\sqrt{2}V_{eq}i_{q,eq} + Q^*\right) &= 0, \\
-\frac{R_f}{L_f}i_{d,eq} + \omega_i i_{q,eq} + \frac{\sqrt{2}}{L_f}(V_{eq} - E \cos \delta_{eq}) &= 0, \\
-\omega_i i_{d,eq} - \frac{R_f}{L_f}i_{q,eq} + \frac{\sqrt{2}}{L_f}(E \sin \delta_{eq}) &= 0, \\
\bar{P}_{eq} - \frac{3}{2}\sqrt{2}V_{eq}i_{d,eq} &= 0.
\end{aligned}$$

### Problem 3.vi

From Eq. 12 and Eq. 7, we get:

$$\begin{aligned}
\dot{i}_d &= f_{i_d} = -\frac{R_f}{L_f}i_d + (\omega_{nom} - m_p(\bar{P} - P^*))i_q + \frac{\sqrt{2}}{L_f}(V - E \cos \delta) \\
\dot{i}_q &= f_{i_q} = -(\omega_{nom} - m_p(\bar{P} - P^*))i_d - \frac{R_f}{L_f}i_q + \frac{\sqrt{2}}{L_f}(E \sin \delta)
\end{aligned}$$

Therefore, the linearized model of Eq. 12 is given as follows:

$$\begin{aligned}
\begin{bmatrix} \Delta \dot{\delta} \\ \Delta \dot{V} \\ \Delta \dot{i}_d \\ \Delta \dot{i}_q \\ \Delta \dot{\bar{P}} \end{bmatrix} &= \begin{bmatrix} \left. \frac{\partial f_{\delta}}{\partial \delta} \right|_{eq} & \left. \frac{\partial f_{\delta}}{\partial V} \right|_{eq} & \left. \frac{\partial f_{\delta}}{\partial i_d} \right|_{eq} & \left. \frac{\partial f_{\delta}}{\partial i_q} \right|_{eq} & \left. \frac{\partial f_{\delta}}{\partial \bar{P}} \right|_{eq} \\ \left. \frac{\partial f_V}{\partial \delta} \right|_{eq} & \left. \frac{\partial f_V}{\partial V} \right|_{eq} & \left. \frac{\partial f_V}{\partial i_d} \right|_{eq} & \left. \frac{\partial f_V}{\partial i_q} \right|_{eq} & \left. \frac{\partial f_V}{\partial \bar{P}} \right|_{eq} \\ \left. \frac{\partial f_{i_d}}{\partial \delta} \right|_{eq} & \left. \frac{\partial f_{i_d}}{\partial V} \right|_{eq} & \left. \frac{\partial f_{i_d}}{\partial i_d} \right|_{eq} & \left. \frac{\partial f_{i_d}}{\partial i_q} \right|_{eq} & \left. \frac{\partial f_{i_d}}{\partial \bar{P}} \right|_{eq} \\ \left. \frac{\partial f_{i_q}}{\partial \delta} \right|_{eq} & \left. \frac{\partial f_{i_q}}{\partial V} \right|_{eq} & \left. \frac{\partial f_{i_q}}{\partial i_d} \right|_{eq} & \left. \frac{\partial f_{i_q}}{\partial i_q} \right|_{eq} & \left. \frac{\partial f_{i_q}}{\partial \bar{P}} \right|_{eq} \\ \left. \frac{\partial f_{\bar{P}}}{\partial \delta} \right|_{eq} & \left. \frac{\partial f_{\bar{P}}}{\partial V} \right|_{eq} & \left. \frac{\partial f_{\bar{P}}}{\partial i_d} \right|_{eq} & \left. \frac{\partial f_{\bar{P}}}{\partial i_q} \right|_{eq} & \left. \frac{\partial f_{\bar{P}}}{\partial \bar{P}} \right|_{eq} \end{bmatrix} \begin{bmatrix} \Delta \delta \\ \Delta V \\ \Delta i_d \\ \Delta i_q \\ \Delta \bar{P} \end{bmatrix} \\
&= \begin{bmatrix} 0 & 0 & 0 & 0 & -m_p \\ 0 & \omega_c - m_q \omega_c \frac{3}{2} \sqrt{2} i_{q,eq} & 0 & -m_q \omega_c \frac{3}{2} \sqrt{2} V_{eq} & 0 \\ \frac{\sqrt{2}}{L_f} E \sin \delta_{eq} & \frac{\sqrt{2}}{L_f} & -\frac{R_f}{L_f} & m_{nom} - m_p (\bar{P}_{eq} - P^*) & -m_p i_{q,eq} \\ \frac{\sqrt{2}}{L_f} E \cos \delta_{eq} & 0 & -(\omega_{nom} - m_p (\bar{P}_{eq} - P^*)) & -\frac{R_f}{L_f} & m_p i_{d,eq} \\ 0 & -\frac{3}{2} \sqrt{2} \omega_c i_{d,eq} & -\frac{3}{2} \sqrt{2} V_{eq} & 0 & \omega_c \end{bmatrix} \begin{bmatrix} \Delta \delta \\ \Delta V \\ \Delta i_d \\ \Delta i_q \\ \Delta \bar{P} \end{bmatrix} \\
&= A \begin{bmatrix} \Delta \delta \\ \Delta V \\ \Delta i_d \\ \Delta i_q \\ \Delta \bar{P} \end{bmatrix}
\end{aligned}$$

#### Problem 4.i

The time domain dynamics of the circuit is given by:

$$\begin{bmatrix} v_t^a \\ v_t^b \\ v_t^c \end{bmatrix} = L \frac{d}{dt} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} + R \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} + \begin{bmatrix} v_0^a \\ v_0^b \\ v_0^c \end{bmatrix}.$$

Converting them to d-q domain (at an angle  $\theta_d = \omega_d t$ ) as illustrated in Q3, we get:

$$\begin{aligned}
\Gamma_{dq}^T \begin{bmatrix} v_t^d \\ v_t^q \end{bmatrix} &= L \frac{d}{dt} \left( \Gamma_{dq}^T \begin{bmatrix} i_d \\ i_q \end{bmatrix} \right) + R \Gamma_{dq}^T \begin{bmatrix} i_d \\ i_q \end{bmatrix} + \Gamma_{dq}^T \begin{bmatrix} v_0^d \\ v_0^q \end{bmatrix} \\
\Rightarrow \Gamma_{dq}^T \begin{bmatrix} v_t^d \\ v_t^q \end{bmatrix} &= L \dot{\theta}_d \Gamma_{dq}^T \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i_d \\ i_q \end{bmatrix} + L \Gamma_{dq}^T \begin{bmatrix} \dot{i}_d \\ \dot{i}_q \end{bmatrix} + R \Gamma_{dq}^T \begin{bmatrix} i_d \\ i_q \end{bmatrix} + \Gamma_{dq}^T \begin{bmatrix} v_0^d \\ v_0^q \end{bmatrix} \\
\Rightarrow \begin{bmatrix} v_t^d \\ v_t^q \end{bmatrix} &= L \omega_d \begin{bmatrix} -i_q \\ i_d \end{bmatrix} + L \begin{bmatrix} \dot{i}_d \\ \dot{i}_q \end{bmatrix} + R \begin{bmatrix} i_d \\ i_q \end{bmatrix} + \begin{bmatrix} v_0^d \\ v_0^q \end{bmatrix}.
\end{aligned}$$

Converting the above equations in block diagrams along with feedback control and following Fig. 3 in the question for point of feed forward, we get the following block diagram shown in Fig. 1 in dq domain as requested in the question.

#### Problem 4.ii

To derive the closed-loop transfer functions  $\frac{i_{dq}(s)}{i_{dq}^*(s)}$ , we need to ignore the cross-coupling terms and  $v_{dc}$  in Fig. 3 (in the question). Then we can get the following the block diagram for  $i_d(s)$  (similar diagram for  $i_q(s)$  too) as shown in Fig. 2:

Considering  $G_c(s) = (k_p + k_i/s)$ , we can derive the transfer function as follows:

$$H(s) = \frac{i_d(s)}{i_d^*(s)}$$

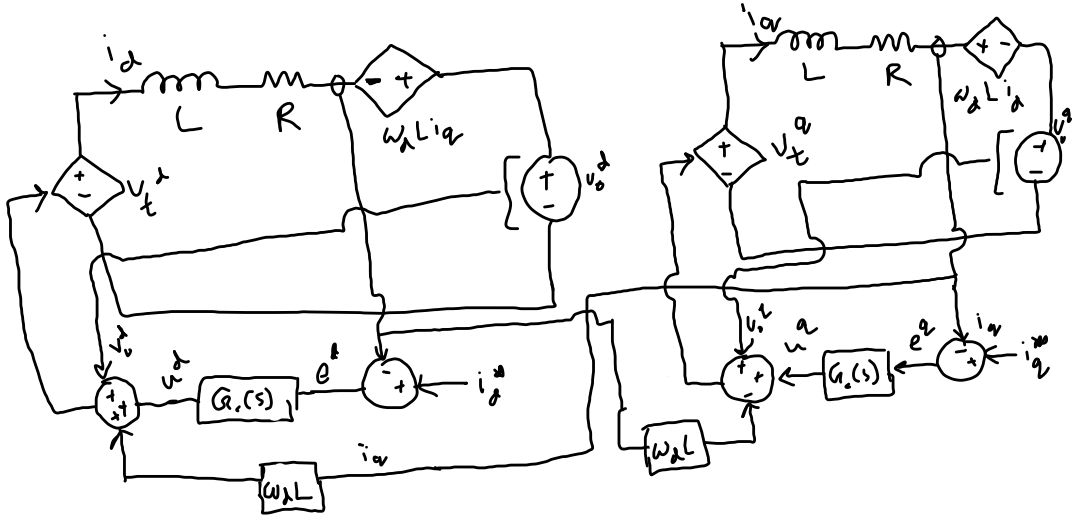


Figure 1: Q4: Inverter feedback control block diagram

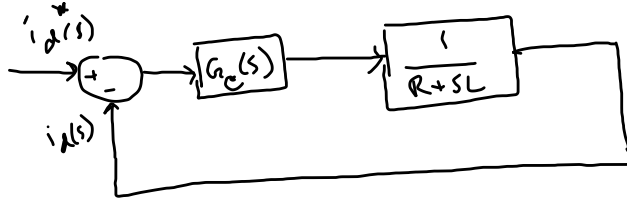


Figure 2: Q4: Block diagram to derive current transfer function

$$\begin{aligned}
 &= \frac{G_c(s)/(R + sL)}{1 + G_c/(R + sL)} \\
 &= \frac{G_c(s)}{(R + sL) + G_c(s)} \\
 &= \frac{k_p + k_i/s}{(k_p + k_i/s) + (R + sL)}.
 \end{aligned} \tag{13}$$

#### Problem 4.iii

From Eq. 13, we get,

$$\begin{aligned}
 H(s) &= \frac{sk_p + k_i}{s^2L + s(R + k_p) + k_i} \\
 &= \frac{1}{\frac{s^2L}{sk_p + k_i} + \frac{s(R + k_p)}{sk_p + k_i} + \frac{k_i}{sk_p + k_i}}
 \end{aligned} \tag{14}$$

Equating denominator of Eq. 14 with that of desired transfer function  $\frac{1}{1 + \tau s}$ , we get:

$$\begin{aligned}
 \frac{s^2L}{sk_p + k_i} + \frac{s(R + k_p)}{sk_p + k_i} + \frac{k_i}{sk_p + k_i} &= (1 + \tau s) \\
 \implies s^2L + s(R + k_p) + k_i &= s^2\tau k_p + s(k_p + \tau k_i) + k_i.
 \end{aligned}$$

Equating corresponding coefficients of  $s$ , we get:

$$L = \tau k_p \implies \tau = \frac{L}{k_p}$$

$$R + k_p = k_p + \tau k_i \implies \tau = \frac{R}{k_i}.$$

Therefore,

$$\begin{aligned} \frac{L}{k_p} &= \frac{R}{k_i} \\ \implies \frac{L}{R} &= \frac{k_p}{k_i}. \end{aligned}$$

Similarly, we can prove the *only if* part as follows.

Let,  $\frac{L}{R} = \frac{k_p}{k_i} = c$ . Also denote  $\tau := \frac{R}{k_i}$ . Then  $\tau = \frac{L}{k_p}$  also. From Eq. 13,

$$\begin{aligned} H(s) &= \frac{k_p + k_i/s}{(k_p + k_i/s) + (R + sL)} \\ &= \frac{1}{1 + \frac{R+sL}{k_p+k_i/s}} \\ &= \frac{1}{1 + \frac{(R/k_i)+s(L/k_i)}{(k_p/k_i)+(1/s)}} \\ &= \frac{1}{1 + \frac{\tau+s\frac{L}{k_p}\frac{k_p}{k_i}}{c+(1/s)}} \\ &= \frac{1}{1 + \frac{\tau+sc\frac{L}{k_p}}{c+(1/s)}} \\ &= \frac{1}{1 + \frac{s\tau+s^2c\tau}{sc+1}} \\ &= \frac{1}{1 + \tau s}. \end{aligned}$$